



Multiplexer and Demultiplexer

Exercises Digital Design


Solution vs. Hints:



While not every response provided herein constitutes a comprehensive solution, some serve as helpful hints intended to guide you toward discovering the solution independently. In certain instances, only a portion of the solution is presented.

1 | MUX - Multiplexer

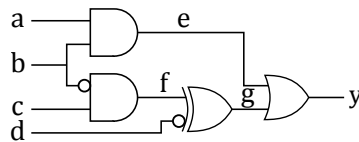1.1 Creating a function with the help of Multiplexers



mux/mux-01



1.2 Creating a function with the help of Multiplexers

| a | b | c | d | y | y' |
|---|---|---|---|---|----------------|
| 0 | 0 | 0 | 0 | 0 | d |
| 0 | 0 | 0 | 1 | 1 | |
| 0 | 0 | 1 | 0 | 1 | \overline{d} |
| 0 | 0 | 1 | 1 | 0 | |
| 0 | 1 | 0 | 0 | 1 | \overline{d} |
| 0 | 1 | 0 | 1 | 0 | |
| 0 | 1 | 1 | 0 | 0 | d |
| 0 | 1 | 1 | 1 | 1 | |
| 1 | 0 | 0 | 0 | 1 | \overline{d} |
| 1 | 0 | 0 | 1 | 0 | |
| 1 | 0 | 1 | 0 | 0 | d |
| 1 | 0 | 1 | 1 | 1 | |
| 1 | 1 | 0 | 0 | 0 | d |
| 1 | 1 | 0 | 1 | 1 | |
| 1 | 1 | 1 | 0 | 1 | \overline{d} |
| 1 | 1 | 1 | 1 | 0 | |

mux/mux-02

1.3 Creating a function with the help of Multiplexers

1.3.1 Solution

- For y 4xMux 2-1
- For z 4xMux 2-1

mux/mux-03

1.4 Creating a function with the help of Multiplexers

- $s = \overline{c}$
- $y = 1$
- $w = \overline{a}$
- ...

mux/mux-04



1.5 Creating a function with the help of Multiplexers

The truthtable non simplified is:

| <i>d</i> | <i>c</i> | <i>b</i> | <i>a</i> | <i>y</i> | <i>z</i> |
|----------|----------|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 1 |

mux/mux-05



2 | MUX - Demultiplexer

2.1 Demultiplexer from 1 to 8

You need 8xAND-4 + 3xNOT

mux/demux-01

2.2 Logic Circuit

You need a XNOR with 2 inputs.

mux/demux-02

2.3 Complete Operators

Multiplexer 2-1 as well as a Demultiplexer 1-2 are both complete operators.

mux/demux-03