

# Introduction to the EDA Tools (IND)

Labor Digital Design

## Contents

1 Objective .....	1
2 Introduction .....	2
3 Combinatorial logic circuit .....	3
3.1 Design .....	3
4 Circuit Editor .....	5
4.1 Components .....	5
4.2 Signals .....	5
4.3 Tasks .....	6
4.4 Layout .....	7
5 Simulation .....	8
5.1 Testbench .....	8
5.2 Simulator .....	8
5.3 Display .....	10
5.4 Glitch .....	11
Bibliography .....	13

## 1 Objective

This first lab is intended to familiarize you with the automated development tools in electronics (Electronic Design Automation (EDA)). You will learn to use the circuit development tool **Mentor HDL-Designer** and the circuit simulator **Mentor Modelsim**, as well as the connection between the two. An example of a simple logic circuit with inverters, AND and OR gates will be created and simulated.



Figure 1: Mentor HDL Designer



Figure 2: Mentor ModelSim




## 2 Introduction

Follow the steps below to download and set up the lab files:

- Download the required lab files via the following [link \(https://github.com/hei-synd-did/did-labs/archive/refs/heads/main.zip\)](https://github.com/hei-synd-did/did-labs/archive/refs/heads/main.zip).
- Unzip the archive on your network drive: \\filer01.hevs.ch\FS\_COURSES\102.1-DiD-102.2-CAR\<firstname.lastname>.
- Run the file **did-labs/did-labs.bat**.



 If a security message appears (*only on the first run*), click on **More Info** and **Run anyways**



- After HDL Designer has opened, click on the **Project** tab.

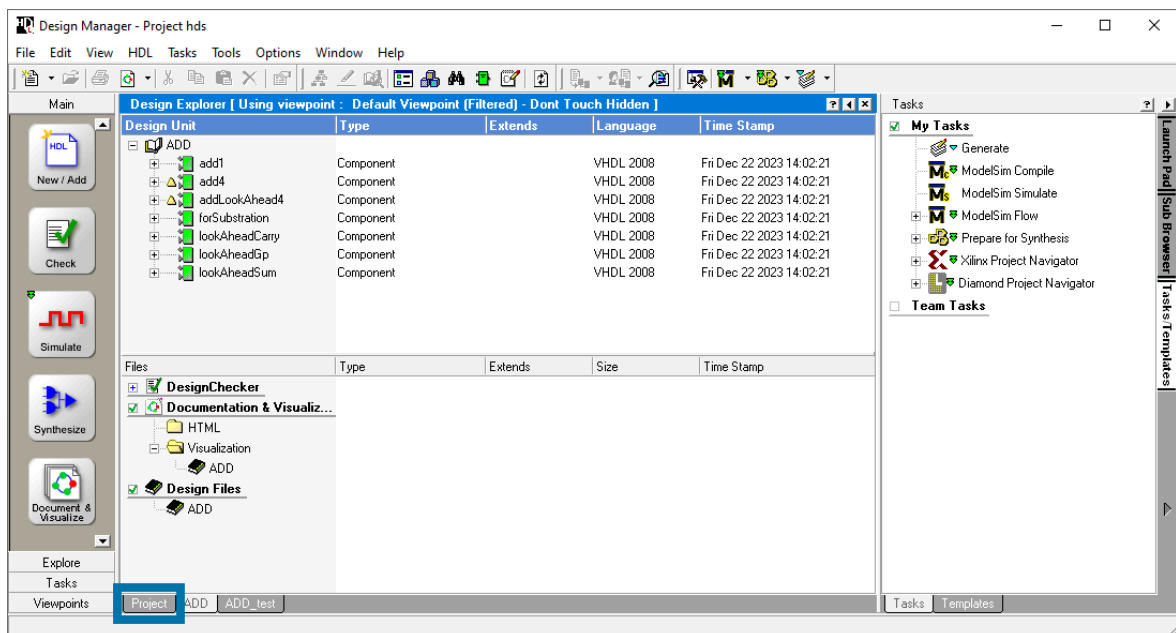


Figure 4: HDL Designer

- Double-click on the relevant libraries for the lab to open them. Each lab has 2 libraries that bear the abbreviation of the lab. In this lab “IND”, they are the **IND** and **IND\_test** libraries.



The files must not be left on the lab computers. They must be saved on a USB stick or on the \\filer01\.... Also share the files with your lab partner so that they can continue the work.



### 3 | Combinatorial logic circuit

We will now move on to the actual circuit that needs to be implemented. A company has decided to check each of its purchases according to strict rules. An item may only be purchased if at least one of the following conditions is met:

- **Condition A:** the company's order books are full, the delivery time of the material is short and the company's stocks are low
- **Condition B:** the order books are not full, but the price and the company's stocks are low
- **Condition C:** the price is high, but the order books are full and the company's stocks are low
- **Condition D:** the company's stocks are low and the delivery time is short
- **Condition E:** the delivery time is long, but the price is low



Complete the truth table [Table 1](#) according to the specification.



Deduce from the table a circuit composed of the basic gates AND, OR and inverter.

#### 3.1 Design

Open the circuit under **IND**  $\Rightarrow$  **selection**. The input and output signals are already defined, as is the condition A (**condition A**).

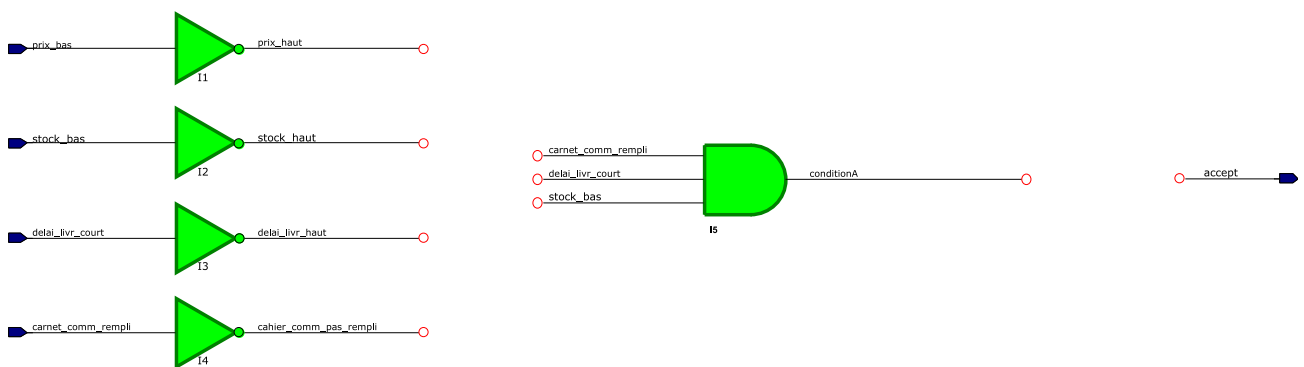


Figure 5: Circuit to complete

[illegible]



## 4 | Circuit Editor

This section will guide you through the creation of a digital circuit.

Using inverters, AND and OR gates, draw the circuit you read from the truth table [Table 1](#).



For detailed information on how to use HDL Designer and ModelSim, refer to the document **DiD-EDA-UserGuide-en.pdf** on Cyberlearn [\[1\]](#).

### 4.1 Components

Components are logical gates, constant signals such as `logic_0` / `logic_1`, multiplexers, flip-flops ... as well as user-created blocks.

- Add a component by clicking on the button **Add Component**.

 


Figure 6: Add Component

- Search for the desired component in the **gates** library.
- Select the component and drag it into the circuit.



Add all components required for your circuit.

### 4.2 Signals

Signals are used to connect the inputs and outputs of the different blocks together. They can represent a bit (**`std_ulogic`**) or several bits (**`std_ulogic_vector`**, **`signed`**, **`unsigned`**). Signals can be connected by lines or by their names.

#### 4.2.1 Adding a Signal

- Add a signal by clicking on the button **Add Signal**.



Figure 7: Add Signal

- After clicking on the button, a new signal can be created by clicking on the schematic.
- To confirm a new signal, connect an input and an output together or double-click to finish creating the signal.
- Press the **ESC** key to cancel the creation of a signal.

#### 4.2.2 Changing the Signal Name

Double-click on a signal to change its name. The name of the signal can be changed in the **text field**.

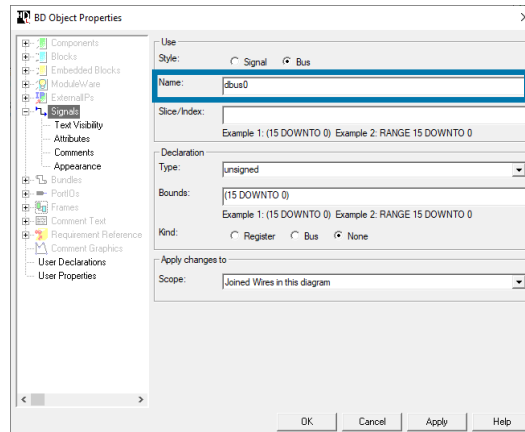


Figure 8: Edit Signal and Bus Properties



Signals with the same name are connected together! Signals with different names must be connected together via buffers.

### 4.3 Tasks

Create your schematic in a clear and readable way.



- Name each signal in the schematic.
- Set the display settings for the signal names.
- Make the schematic readable by connecting some signals by name and not by a wire.



It is important to always display the name of a signal. Incorrect manipulation sometimes changes the name automatically and this is not detectable without the signal name.



## 4.4 Layout

The circuit, once properly filled out, can be printed and/or exported as a PDF.

First:



Fill in the available frame.



Make all necessary changes to make this circuit as readable as possible.

To create the PDF or print, go to **File** ⇒ **Page setup** and use the following configuration:

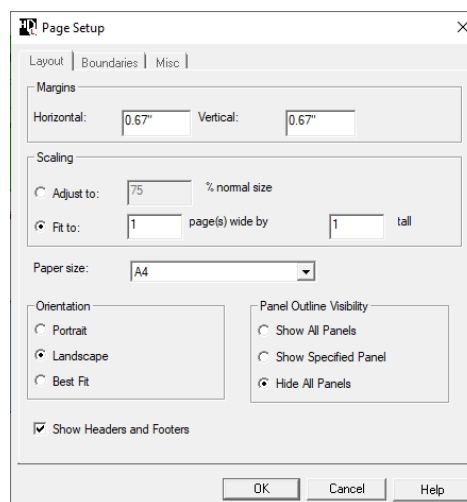


Figure 9: Page configuration

- Print the circuit on a physical printer or select **Adobe PDF** or **Microsoft print to PDF** to export the page as a **PDF**.



Export your circuit as a PDF.



## 5 | Simulation

To ensure that the circuit works correctly, a simulation is performed testing all possible combinations of input signals.

### 5.1 Testbench

The simulation is located under **IND\_test**  $\Rightarrow$  **IND\_tb**.

The **Testbench** is composed of two parts:

- The circuit to be tested (**DUT - Device Under Test**), the circuit developed previously
- The tester generating the input signals for the DUT and checking the outputs.

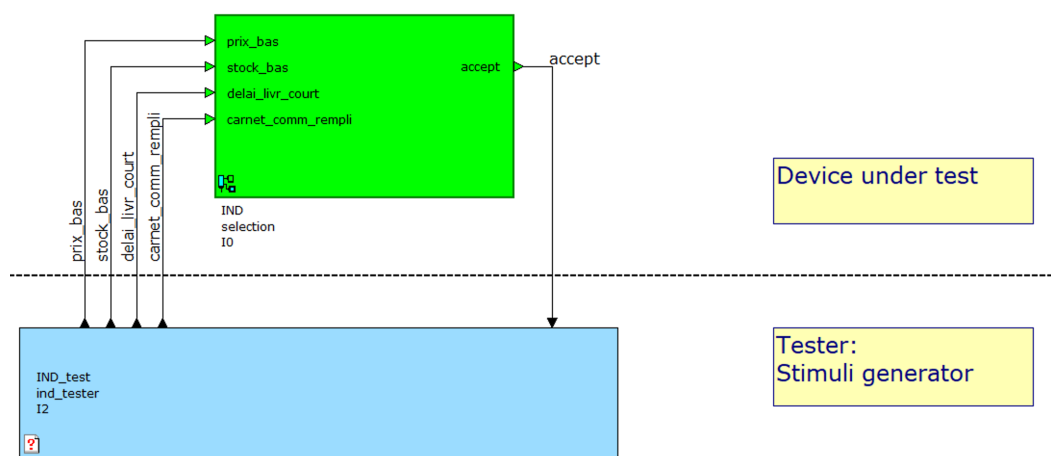


Figure 10: Generate VHDL

### 5.2 Simulator

Click on the button **Generate and run entire ModelSim flow (Through Components)** to start the simulation.

 


Figure 11: Generate VHDL



When the simulation is started, no block of the circuit must be selected.

- If the generation and compilation are successful, the following window will appear:






- ▶ Enter the **initialization command file (\*.do)**, in this case **\$SIMULATION\_DIR/IND.do**. This file contains the information of the signals to be displayed.
- ▶ Click on **OK**.



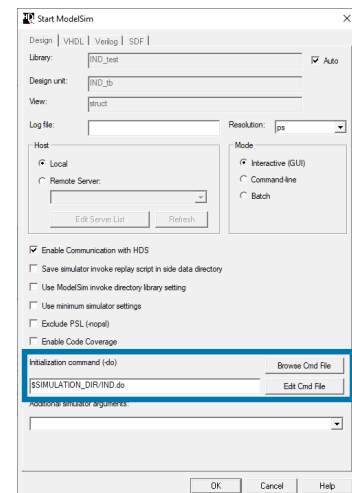The \*.do files are located in the **Simulation** directory, located at the root of **did-labs**.



If nothing happens when the simulation is started, check the log window. If the log window is not displayed:

- Right-click on the **Log Window** window.
- Click on **Maximize**.

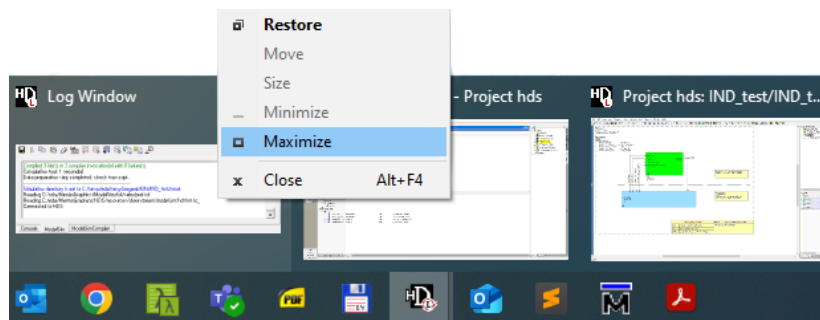


Figure 12: Display the log window

This window displays problems related to the compilation of the circuit that must be corrected to start the simulation.

Errors can be displayed in **Red**, **Green** or **Black**.



Start the simulation program using the file **\$SIMULATION\_DIR/IND.do**.

### 5.2.1 Starting the simulation

The simulation is “stimulated” by the tester block with values.



Open the testers file and determine the required simulation time.



- Enter the simulation time in the **Text field**.
- Click on the button **Start simulation**.
- With the button **Reset simulation** you can reset the simulation.



Start the simulation and check if the input and output signals are correct.

## 5.3 Display

The different elements of the simulation program **Mentor ModelSim** are shown in [Figure 13](#):

 


Figure 13: Simulation with only condition A

1. Hierarchy of the circuit, of each individual block window **1**. By selecting a block, the associated signals are displayed in window **2**.
2. Displays the available signals in the selected block. They can be dragged into window **3** (Drag&Drop) to display them.
3. The **Wave** simulation window with the signals of the circuit.

### 5.3.1 Adding signals

Adding signals is done as described previously.

After adding signals, a restart of the simulation is necessary to display them.



Add the signals of the remaining 4 conditions in the simulation window.

### 5.3.2 Time scale

By right-clicking on the time scale ⇒ **Grid, Timeline & Cursor control** you can change the time scale and the time marking grid.



Change the time scale to be displayed in nanoseconds.

### 5.3.3 Functionality control

To check the functionality of the circuit, the signals must be correlated with each other.



In some labs, the **Transcript** window at the bottom of **ModelSim** can also display information about automated tests.



Check if your simulation matches your truth table [Table 1](#).

### 5.3.4 Saving the context

To be able to reopen the simulation with the previous settings, you can save the configuration by pressing **Ctrl + s** in the **Wave** window.

The generated **.do** file can be saved in the **Simulation** folder of the project.



Save the configuration of the simulation and overwrite the current file **IND.do**.

### 5.3.5 Printing the simulation

Like the schematic, simulation signals can be printed or exported as PDF via **File** ⇒ **Print....**

A recommended print configuration is shown in [Figure 14](#):

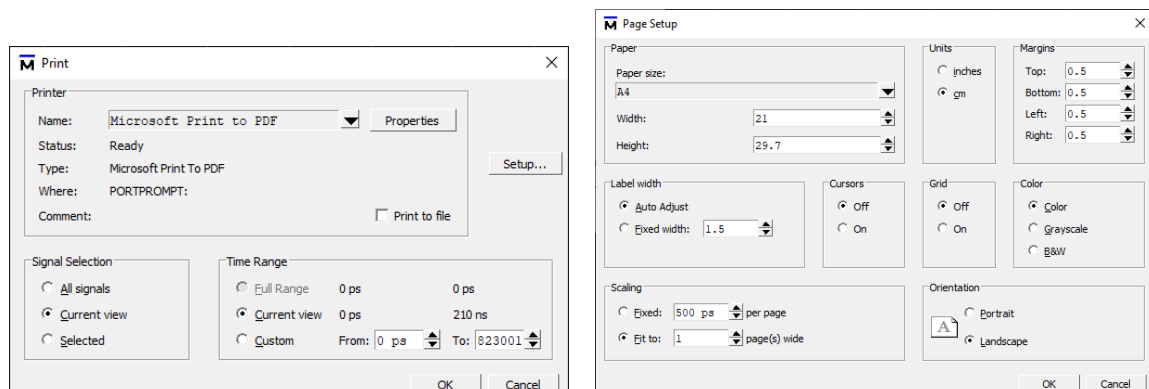


Figure 14: Recommended print configuration for the simulation



Export the result of the simulation as PDF.

## 5.4 Glitch

Glitches can appear on the output signal. One of these glitches is highlighted in [Figure 15](#).

 


Figure 15: Glitch on the output signal



- Find these glitches in your simulation.
- Explain the reason for these glitches.



# Bibliography

- [1] A. A. Silvan, Zahno Rémy, Borgeat, “DiD EDA Userguide.” 2024.